

## 1. General

$10^{\pm}$	21	18	15	12	9	6	3	2	1
+	Z zetta	E exa	P peta	T tera	G giga	M mega	k kilo	h hecto	da deca
-	z zepto	a atto	f femto	p pico	n nano	$\mu$ micro	m milli	c centi	d deci

## 2. SoC Paradigm

### 2.1. Moore's Law


Chip capacity (transistors, performance) doubles every 18–24 month

### 2.2. Challenges

**Optimization:** Time-To-Market, Price, Performance, Power Cons.  
**Productivity:** reuse components, shorter development cycles, higher chances for (first time) fault-free design

### 2.3. Chip Platforms


Platform	CD	FC	units	costs
CPU	40 – 80	256 – 16k	ALU	very few
DSP			Multiplier	few
ASIP			special exec units	thousands
FPGA	400	1	LUTs	millions
ASIC	4 000	10	standard cells	10 millions
Cust. IC	> 10 000	≈ 0	transistors	

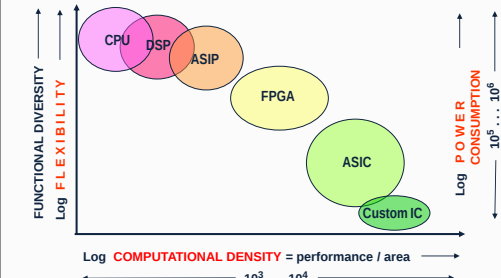

$CD = \frac{IPC \cdot f \cdot w \cdot \lambda^2}{A}$   
 Instructions per cycle IPC, structure size  $\lambda$ , area  $A$   
 Frequency  $f$ , Wordsize  $w$  (e.g. 32 Bit)
 
### 2.4. CMOS


Complementary Metal (Poly-Si) Oxide (SiO<sub>2</sub>) Semiconductor  
 Why? Low power dissipation, Noise immunity, Clean logic levels, One supply voltage, Cascadable, Easy to design, Fabrication well understood



### 2.5. MOSFET


channel width	$W_{n/p}$
channel length	$L_{n/p}$
gate oxide thickness	$t_{ox}$
electron mobility	$\mu_n \approx 250 \times 10^{-4} \frac{m^2}{Vs}$ $\mu_p \approx 200 \times 10^{-4} \frac{m^2}{Vs}$
rel. permittivity of gate oxide	$\epsilon_{ox} \approx 3,9$
dielectric constant	$\epsilon_0 = 8.854 187 8 \times 10^{-12} \frac{As}{Vm}$
specific oxide capacity	$C'_{ox} = \frac{\epsilon_{ox} \epsilon_0}{t_{ox}}$
oxide capacity	$C_{ox} = C'_{ox} \cdot WL$
gain (also $\beta$ )	$K_n = \mu_n C'_{ox} \frac{W_n}{L_n}$ $K_p = (-1) \mu_p C'_{ox} \frac{W_p}{L_p}$
propagation delay	$t_{pHL} \propto \frac{C_L t_{ox} L_p}{W_p \mu_p \epsilon_{ox} (V_{DD} -  V_{th} )}$

### 2.6. Inverter

 

## 3. SoC Components

### 3.1. Sequential Logic

 


$t_{Setup}$	setup before clock edge
$t_{hold}$	hold after clock edge
$t_{c2q}$	output valid after $t_{c2q}$
Max. clock period	$t_{clk} \geq t_{1,c2q} + t_{logic,max} + t_{2,setup}$
Max. clockfrequency	$f_{max} = \lfloor \frac{1}{t_{clk}} \rfloor$ (Nicht aufrunden)
hold time condition	$t_{hold} \leq t_{c2q} + t_{logic,min} \rightarrow$ Dummy Gate
Durchsatz	$\frac{1}{t_{clk,pipe}} = f$
Latenz	$t_{clk} \cdot \# \text{Pipeline stages} (\#FFs - 1)$
Slack	$t_{slack} = t_{available} - t_{required}$

### 3.2. Karnaugh-Maps


$\sum^{xy}$	00	01	11	10	
0	1	0	0	0	Combine equal cells: e.g. $\bar{x}y + y \cdot z$ Use don't care values!
1	X	1	1	0	

### 3.3. Finite State Machines

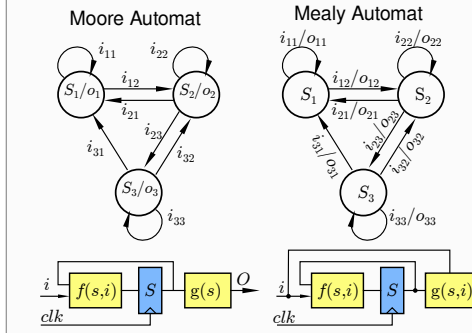

Synchronous System Design paradigm: Essentially all control functions in state-of-art digital IC's consist of "communicating FSM's".  
 Avoid combinatorial logic through paths!  
 Stick to one FSM design style across SoC!

### 3.4. Adder

 

#### 3.4.1 Ripple-Carry

Worst-Case ( $G, P = 1$ ):  $t_{add} = (N - 1)t_{carry} + t_{sum}$   
 Number of input Bits/Full Adders  $N$

#### 3.4.2 Carry-Bypass

Fast carry propagation (useful if  $N > 4$ )  
 $t_{CBA} = t_{setup} + B t_{carry} + (\frac{N}{B} - 1) t_{skip} + (B - 1) t_{carry} + t_{sum}$   
 switch group size in bits  $B$ .  $t_{CBA}$  still  $O(N)$ , but with more graduate slope

#### 3.4.3 Carry-Select

Precompute  $C_{out}$  for  $C_{in} = 0$  and  $C_{in} = 1$  for all blocks in parallel. Then select the correct one.  $t_{CSA} = t_{setup} + B t_{carry} + \frac{N}{B} t_{mux} + t_{sum}$   
 Square Root Carry-Select Adder:  
 $t_{SCS} = t_{setup} + M t_{carry} + \sqrt{2N} t_{mux} + t_{sum}$


### 3.5. Multiplier (Addition of partial products)

$$x \cdot y = \sum_{j=0}^{M-1} \sum_{i=0}^{N-1} x_i y_j \cdot 2^{i+j}$$

Result requires  $N + M$  bit

#### 3.5.1 Repeated Addition
 
#### 3.5.2 Sequential: Right Shift and Add



#### 3.5.3 Array Multiplier

All partial products generated in parallel and organized in adder array with respective offset  
 $t_{mul} = [(M - 1)(N - 2)]t_{carry} + (N - 1)t_{sum} + t_{and}$

### 3.6. Shifter

Single-bit left/ right shift operations through individual pass transistors  
 Barrel Shifter: Words pass through maximum one transmission gate

### 3.7. Multiplexer


Mux:  $Z = \bar{S}A_1 + SA_1$     DeMux:  $Z_1 = \bar{S}A, Z_2 = SA$

## 4. Processor Structure

### 4.1. Processor Classification

	Type	Application	Characteristic	Remark
Instruction complexity	RISC	Embedded control	Load/store instructions for memory access	MIPS, ARM, PowerPC
	CISC	Personal Computer/ Servers	Complex, variable-length instructions	Intel x86-based
Instruction-level parallelism (ILP)	Superscalar	Personal Computer/ Embedded	Instruction parallelism on run-time	Intel, ARM, PowerPC
	VLIW	Image Processing	Instruction parallelism on compile-time	Parallel video pixel processing
Application-specific area	ASIP	Embedded	Application-specific instructions	Tensilica
	DSP	Signal Processing	HW multiply for digital filters	TI

### 4.2. Software Levels

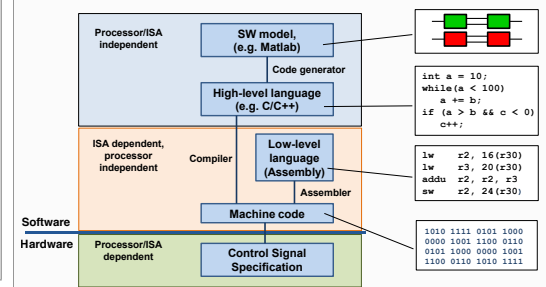


### 4.3. Multi Cycle Core

1. Instruction Fetch (IF): increase PC
2. Instruction Decode (ID): read OP and register
3. Execution (EX): ALU executes command
4. Memory Stage (M): read/write to memory
5. Write Back (WB): load from memory to register?

 
#### 4.4. Hazards (problems due to pipelining)

**Structural Hazard:** same resource is needed multiple times in the same cycle



**Data Hazard:** data dependencies (read-after write, write-after-write, write-after-read).

 Solution: Forwarding, Stalling, Scheduling




Stalling is required



With register forwarding: Only 1 stall below EX.

**Control Hazard:** next executed instruction is not the next specified instruction due to jump, branch, exception.

Solution: Branch predictor

 


#### 4.5. Processor Performance

$$\text{CPU Time} = \frac{\text{Instructions}}{\text{Program}} \cdot \frac{\text{Clock Cycles}}{\text{Instruction}} \cdot \frac{\text{Seconds}}{\text{Clock Cycle}}$$

Estimate                      CPI                       $\frac{1}{f_{\text{CPU}}}$

#### 5. Memory

 


Type	Used	Speed	Density
Register	CPU Registers	< ns	32 · 64 bit
On-Chip SRAM	Cache	ns	32 kByte
DDR3 SDRAM	Main Memory	2 · 800 MHz	≈ GByte
HDD	Mass Storage	150 $\frac{\text{MB}}{\text{s}}$	> TB
ROM	Sys. Config	≈ kB/s	few kByte

#### 5.1. CMOS Memory

Register: 2 Inverters (Q,  $\bar{Q}$ )  
Latch: 4 NANDS (e, D, Q,  $\bar{Q}$ )  
Flip-Flop: (Q,  $\bar{Q}$ , clk)
 
#### 5.2. Cache


Caches store only small share of main memory. The Cache maps RAM-Addresses to Cache-Entries. One Cache-Entry can contain several Data Bytes. The Tag verifies the mapping, the Valid-Flag verifies the actuality of the cached data.



#RAMAddressBits = #TagBits + #IndexBits + #OffsetBits  
#CacheEntries =  $2^{\text{Indexbits}}$   
#CacheDataBytes =  $2^{\text{Offsetbits}}$  (Byte accurate Cache access)  
CacheSizeInByte = #CacheEntries · #CacheDataBytes

#### 5.2.1 Direct Mapped Cache

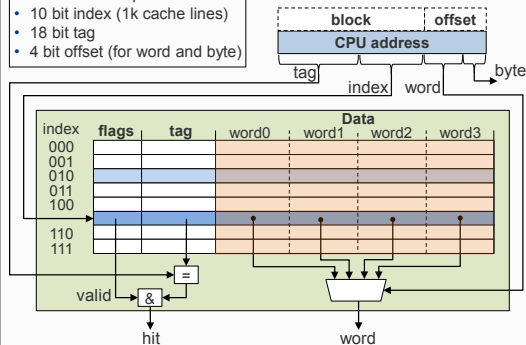Example: 16 KB direct mapped  
4 words à 32 bit per cache line  
• 10 bit index (1k cache lines)  
• 18 bit tag  
• 4 bit offset (for word and byte)



Replace Strategy: Replace old with new.

#### 5.2.2 Set-Associative-Cache


Blocks with equal Index can be stored in  $n$  cache entries. Tag needed to distinguish. Replace Strategy: Replace if all sets are full. Random, FIFO or LRU (least recently used)

$$\frac{\#Zugriffe}{\text{Zeit}} = \text{Hit-Rate} \cdot \text{Hit-Time} + \text{Miss-Rate} \cdot \text{Miss-Time}$$


#### 5.2.3 Fully Associative Cache

A memory block can be stored in any cache entry.

#### 5.3. Branch Prediction

 


#### 5.4. Main Memory

 

$$\Delta V = (V_X - V_{Pre}) \cdot \frac{C_S}{C_S + C_{BL}} \quad V_{Pre} \approx 0.5 V_{DD}$$


$$\Delta V_{BL} = V_{eq} - V_{BL} = \pm \frac{C_S}{C_S + C_{BL}} \cdot \frac{V_{DD}}{2}$$

#### 5.5. Memory Block

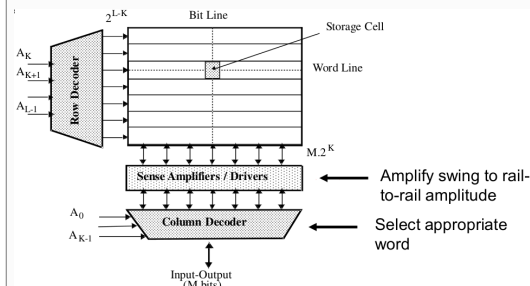


#### 5.6. Memory cell types


##### DRAM

 

##### SRAM

 

##### Flash

 

DRAM Timings:  $t_{CAS} - t_{RCD} - t_{RP} - t_{RAS}$   
Access Latency:  $t_{Lat} = t_{CAS} + t_{RCD}$   
Min. row cycle:  $t_{RC} = t_{RP} + t_{RAS}$


Access Times:  
DRAM: Single:  $(cLatency + 1c(amp)) \cdot \#reads$   
Burst:  $cLatency + (\#reads-1) + 1c(amp)$   
SRAM: Single:  $cLatency \cdot \#reads$   
Burst:  $cLatency + (\#reads-1)$

### 6. Interconnect

#### 6.1. Interconnection
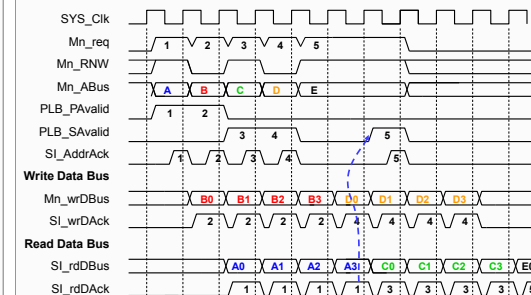
##### 6.1.1 Processor Local Bus (PLB)

Bus-Transaction: Request → Addr. Trans. → Data Trans. → Data Ack  
Burst Transfer: Reduction of Req./Addr. signaling overhead for read/write transactions to consecutive addresses. Burst transfers with implicit address increment



Bus Standard: AMBA (ARM), CoreConnect (IBM), OCP (Sonics), VSIA

#### 6.2. AMBA AHB

Advanced Microcontroller Bus Architecture Advanced eXtensible Interface

#### 6.3. FIFOs

Are use for decoupling clock domains or word widths.  
Pointer: Read (RP) and Write (WP)  
Control Flags: Almost Full (AF) and almost empty (AE)

#### 6.4. Network-on-Chips (NoC)

Benefits: Scalability, Synchronization, short point-to-point links  
Drawbacks: Latency, Area

### 7. Low Power Design

#### 7.1. Motivation – Why?

- Reliability: Plus 10°C doubles failure rate
  - High currents destroy on-chip wires
  - Cooling: higher costs and power consumption
- Leakage current:  $I_{leak} \propto \exp(V_{GS} - V_{th})$   
Gate Delay:  $t_d \propto \frac{C_L}{V_{DD} - V_{th}}$

#### 7.2. Techniques and Hierarchy

Trade in Power with Performance, Area, Cost

Frequency Scaling and Voltage Scaling (DFS, DVS)  
Algorithmic Optimization:  $x^2 + ax = x(x + a)$   
Power Gating: Switch components off if not needed.  
**Clock Gating:** toggle registers only when outputs can change  
Threshold Control: bias threshold voltage  $V_{th}$